LESSON 3 – PERFORM STARTING SYSTEM DIAGNOSIS

INTRODUCTION

A faulty starting system doesn't always mean the starter motor itself is the issue. A proper diagnosis involves checking the entire starting circuit, including the battery, solenoid, cables, switches, and electronic control units. This lesson teaches how to systematically identify faults using tools like a multimeter, amp clamp, and OBD-II scanner to avoid guesswork and costly part replacements.

© LEARNING OBJECTIVES

By the end of this lesson, students should be able to:

- I. Identify common symptoms and causes of starting system problems.
- 2. Use diagnostic tools, including multimeters and OBD-II scanners.
- 3. Interpret voltage, current, and code readings to isolate faults accurately.

SECTION I: COMPONENTS OF THE STARTING SYSTEM

- Battery
- Ignition switch
- Starter relay / solenoid
- Starter motor
- Ground/power cables
- ECU/immobilizer (in modern vehicles)

Any failure in this chain can prevent the engine from starting.

SECTION 2: COMMON SYMPTOMS & CAUSES

Symptom	Possible Cause
No crank, no click	Dead battery, faulty ignition switch
Clicks only	Weak battery, bad solenoid
Slow crank	Corroded terminals, poor ground
Crank but won't start	Not a starting issue—fuel or spark fault
Starts intermittently	Faulty switch, relay, or control module

SECTION 3: DIAGNOSTIC TOOLS

Tool	Use
Multimeter	Voltage, resistance, continuity checks
Battery tester	Battery health and load test
Amp clamp	Measure starter current draw
Test light	Check power at terminals
OBD-II scanner	Read electronic fault codes (DTCs)

SECTION 4: DIAGNOSTIC PROCEDURE

- Step I: Visual Inspection
 Check for loose or corroded terminals
 Ensure battery cables are tight and clean
 - Step 2: Battery Voltage TestMultimeter should read ≥ I 2.6V at restDuring cranking: should not drop below 9.6V

SECTION 4: DIAGNOSTIC PROCEDURE

Step 3: Check Voltage at Starter
Probe the starter terminal during crank
If power is present but no crank → bad starter
If no power → check relay, ignition switch, or wiring

Step 4: Voltage Drop Test

Positive side: <0.5V

Ground side: <0.2V during cranking

High readings = corroded or damaged cables

Step 5: Amp Draw Test

Normal draw: 125-250 amps (depending on engine size)

High draw + no crank = starter motor binding

Low draw = weak battery or high resistance

SECTION 5: USING AN OBD-II SCANNER FOR DIAGNOSIS

In modern vehicles, the ECU stores fault codes related to:

- Starter relay
- Ignition switch
- Immobilizer or anti-theft system
- Low voltage or starter circuit failure

Steps:

- I. Connect scanner to OBD port
- 2. Turn ignition ON (don't crank)
- 3. Scan for DTCs (e.g., P0615 Starter Relay Malfunction)
- 4. Use codes + live data to check starter request status
- OBD-II tools enhance diagnostic accuracy, especially on push-start vehicles or newer models with electronic start controls.

TROUBLESHOOTING MATRIX

Issue	Likely Fault
No crank, all lights OK	Faulty starter or relay
Click but no spin	Bad solenoid or internal starter fault
Engine starts then dies	Immobilizer or ECU issue
Cranking is weak or slow	Battery or high cable resistance

RECOMMENDED VIDEO TUTORIAL

Video: How to Diagnose Starting System Problems
 YouTube Channel: ProDemand Training

https://www.youtube.com/watch?v=sfuEKQBWsIc

Shows:

Live system diagnosis
Use of multimeter & scanner
Fault isolation techniques



LESSON SUMMARY

- A good diagnosis checks electrical and electronic components
- Combine visual checks, electrical testing, and OBD code scanning
- High resistance, weak batteries, or ECM faults can all mimic starter issues
- Always follow a step-by-step test flow to avoid misdiagnosis

REFERENCES

- Auto Electrical System Module TESDA Learning Material https://www.scribd.com/document/601714455/Auto-Electrical-System-Module-PDF
- TESDA Training Regulations Automotive Servicing NC II https://www.tesda.gov.ph
- YouTube ProDemand Training
 How to Diagnose Starting System Problems
 https://www.youtube.com/watch?v=sfuEKQBWslc